

Intro. to the Smith Chart


Transmission Line Applications

Background

- Philip Smith of Bell Laboratories developed the “Smith Chart” back in the 1930”s to expedite the tedious and repetative solution of certain rf design problems. These include:
 - Transmission line problems
 - Rf amplifier design and analysis
 - L-C impedance matching networks
 - Plotting of antenna impedance
 - Etc.


CONSTRUCTION

- The Smith Chart is made up of a family of circles and a second family of arcs of circles.
- The circles are called “constant resistance circles”
- The arcs are “constant reactance circles”
- Impedances must be entered in rectangular form – broken down into a real and an imaginary component.
- The real part (resistance) determines the circle to use.
- The imaginary part (reactance) determines the arc to use.
- The intersection of an arc and a circle represents the plotted impedance.

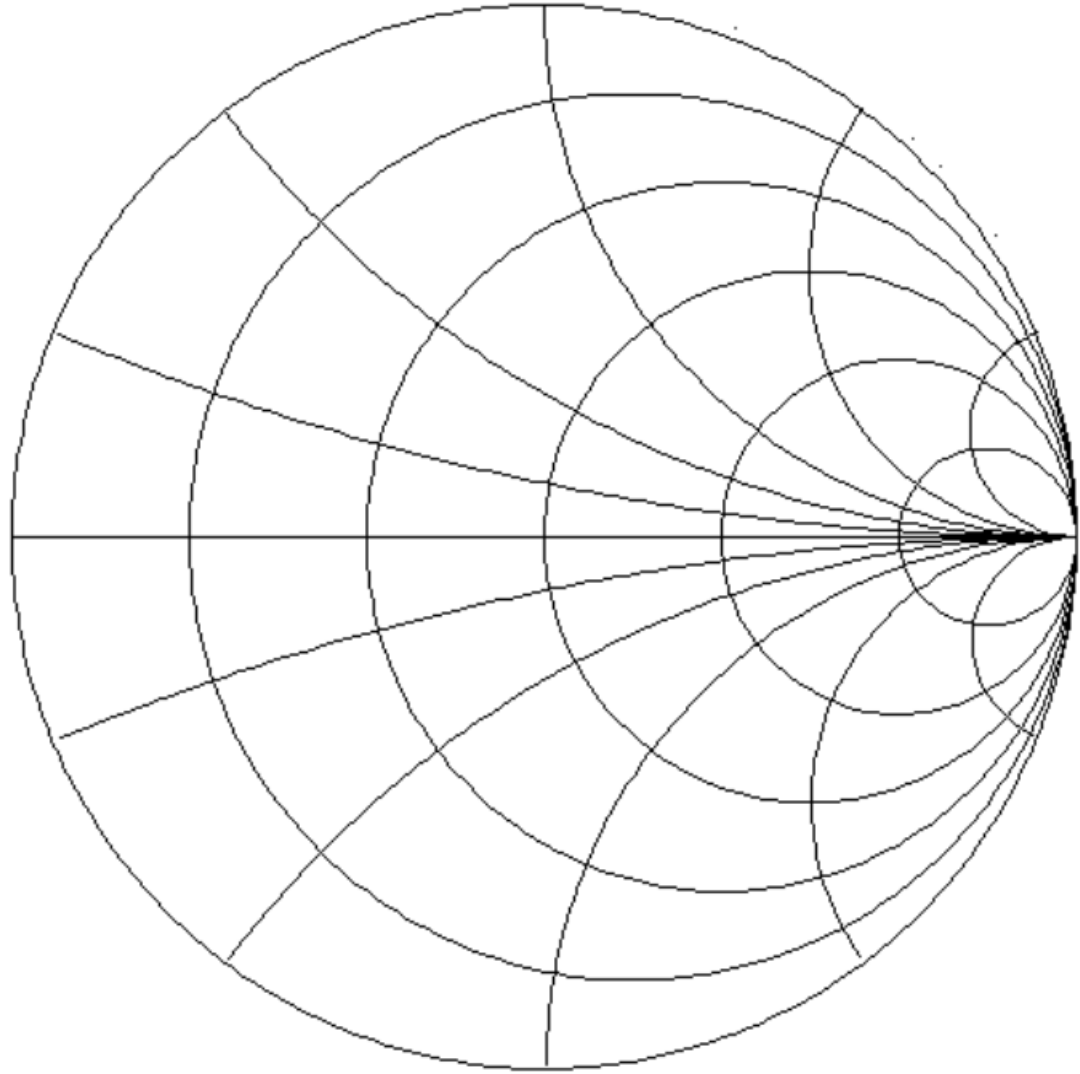

The Complete Smith Chart

Black Magic Design

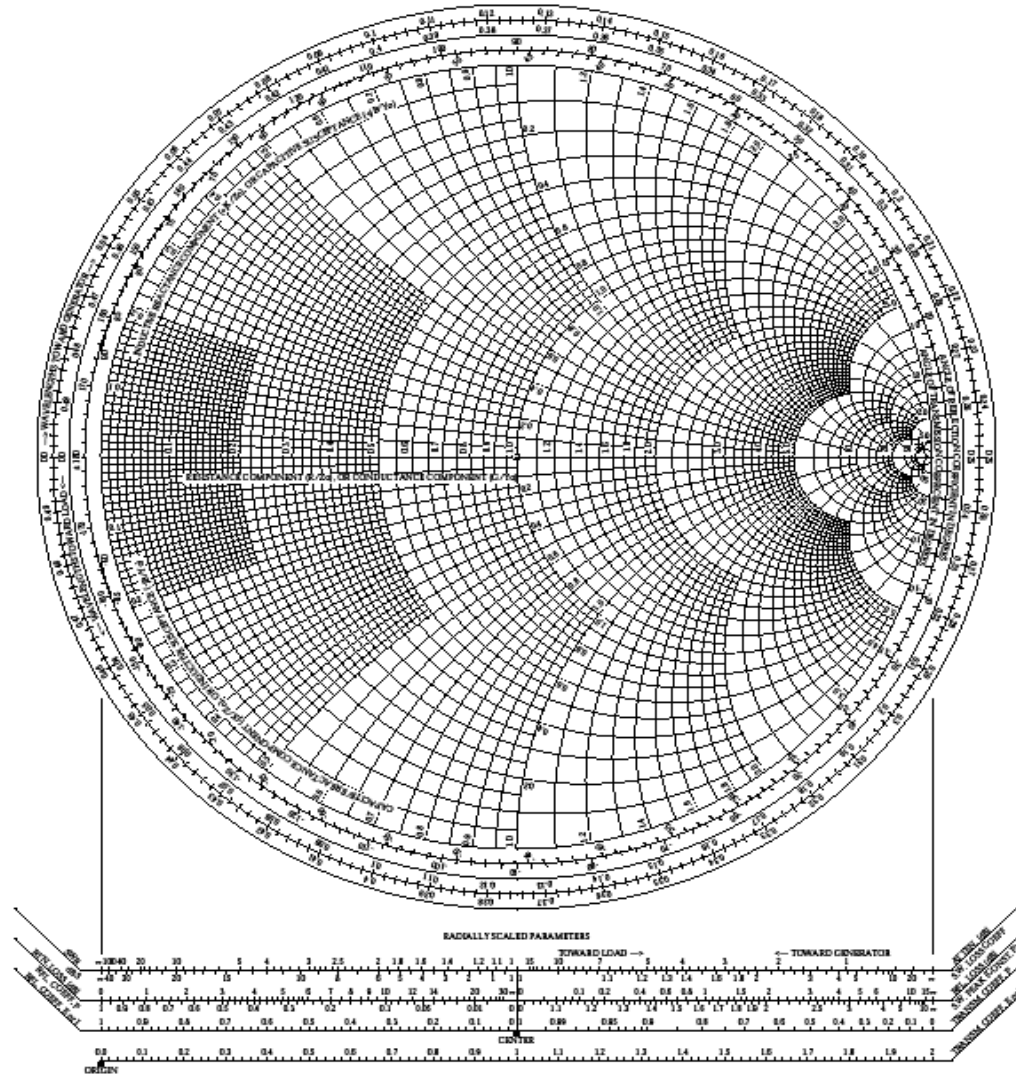

Antenna Z known, find Z at transmitter

Assume an antenna impedance (Z_L) of $25 + j50$ ohms

Let characteristic impedance of the transmission line = 50 ohms

Let velocity factor of cable (vf) = 0.66

Let physical line length = 100 feet = 30.48 meters

Let the frequency (f) be 14.1 MHz

One electrical wavelength on cable = $(983.6)(vf)/f(\text{MHz}) = (983.6)(.66)/14.1 = 46.04$ ft.

Wavelength of actual cable = $100 \text{ ft.}/46.04 \text{ ft.} = 2.172$ wavelengths or 781.9 degrees

Subtract 0.5 wavelengths until the result is less than or equal to 0.5 wavelengths.

The length to plot is 0.172 wavelengths or 61.9° (toward source).

Normalize Load Z


- Since the cable impedance is 50 ohms, we must divide the load impedance by 50 to plot it on the Smith Chart.
- Z_L (normalized) = $(25 + j50)/50$
- $= 0.5 + j1.0$

Plotting

- Place a dot at $0.5 + j1.0$
- Extend a radial line from the center through $0.5 + j1.0$ to the “wavelengths toward generator” scale on the periphery.
- Read approx. 0.1345
- Add 0.172 to get 0.3065
- Extend another radial line from the center through 0.3065 on the “wavelengths toward generator” scale.



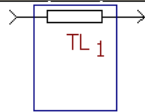Z: -12.85,16.53
Y:0.0293,-0.0377
S: 4.07<141.27
G: 1.60<141.27
V: -4.34



Part Values:


Length (deg):	61.9
Zo (ohm):	50
Freq (MHz):	14.1
Atten (dB):	1e-20

Sweep Range:

Lower Freq (MHz):	14.1
Upper Freq (MHz):	14.1
Sample Points:	1

Terminations:


Reference (ohms):	50
Load R (ohms):	25
Load X (ohms):	50

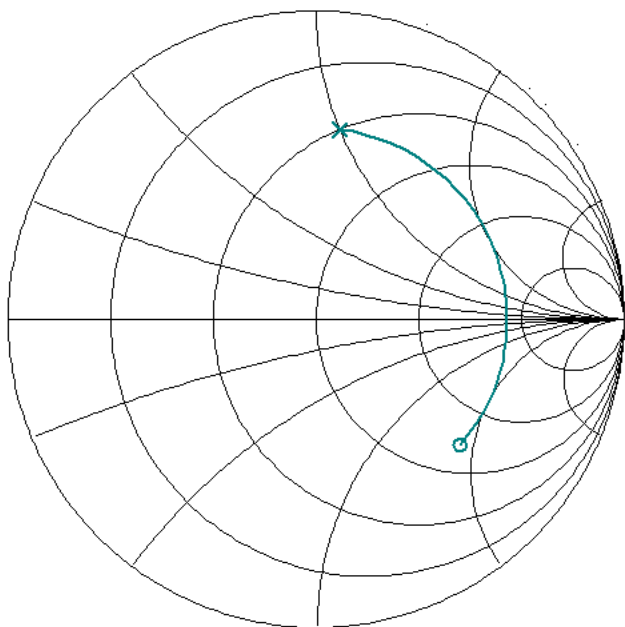

TUNE: 5% Enter the characteristic impedance in ohms for TL1.

Plotting Cont'

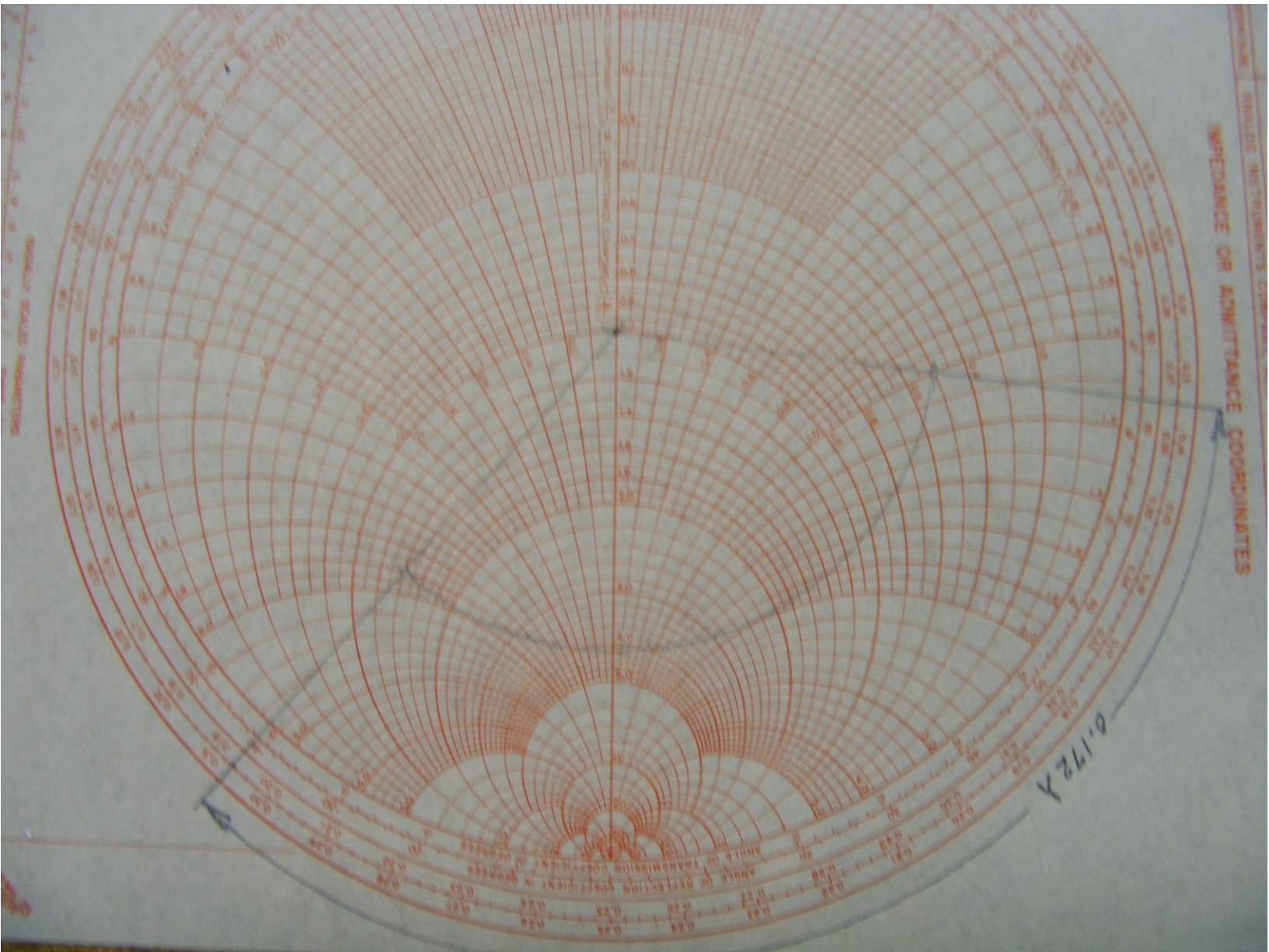- Place one leg of your dividers on the center and the other leg on $0.5+j1.0$
- Draw an arc clockwise (0.172 wavelengths) to the second radial.
- Read approx. $1.4 - j1.8$ at the intersection.
- Multiple by 50 to un-normalize.
- Z at sending end is approx. 70-j90 ohms
(An inductive antenna impedance looks capacitive at the transmitter.)



IMPEDANCE OR ADMITTANCE COORDINATES

0.172λ

TLW, Transmission Line Program for Windows

Help

Version 2.0, Copyright 2000-2003, ARRL, by N6BV, July 22, 2003



Cable Type:

- Feet
- Meters

Length: Feet Lambda Frequency: MHz

Use "w" suffix for wavelength (for example, 0.25w)

Characteristic Z0: 50.0 - j 0.00 Ohms Matched-Line Loss: 0.0 dB/100 Feet

Velocity Factor: 0.66 Max Voltage: 100 V Total Matched-Line Loss: 0.000 dB

Source

- Normal
- Autek
- Noise Bridge

- Load Resistance: Ohms
- Input Reactance:

- Volt./Current
- Resist./Reac.

Graph

Tuner Print Exit

SWR at Line Input: 4.27 SWR at Load: 4.27 Rho at Load: 0.62017

Additional Loss Due to SWR: 0.000 dB Total Line Loss: 0.000 dB

Impedance at Input: 68.60 - j 90.72 Ohms = 113.74 Ohms at -52.90 Degrees

Input Impedance (Z_{in}) of a lossless transmission line :

$$j := \sqrt{-1} \quad \text{define "j"}$$

Problem parameters:

$$l := 100\text{ft}$$

$$\phi := 61.9\text{deg}$$

$$Z_o := 50$$

$$Z_L := 25 + 50j$$

$$Z_{in} := Z_o \cdot \frac{\left[\left(\frac{Z_L}{Z_o} \right) \cdot \cos(\phi) + j \cdot \sin(\phi) \right]}{\cos(\phi) + j \cdot \left(\frac{Z_L}{Z_o} \right) \cdot \sin(\phi)}$$

Answer:

$$Z_{in} = 68.766 - 90.794i$$

OHMS